

ORDRE DES INGÉNIEURS DU QUÉBEC

NOVEMBER 2019 SESSION

Open-book examination  
Calculators : only authorized models  
Duration : 3 hours

16-EL-A1-CIRCUITS

**Question 1 (10 points)**

Considering that the operational amplifiers of the circuit shown in Figure 1 are ideal and operate in the linear area,

- Find the output voltage,  $v_o$ .
- Give the power dissipated through the  $4\text{k}\Omega$  resistor.

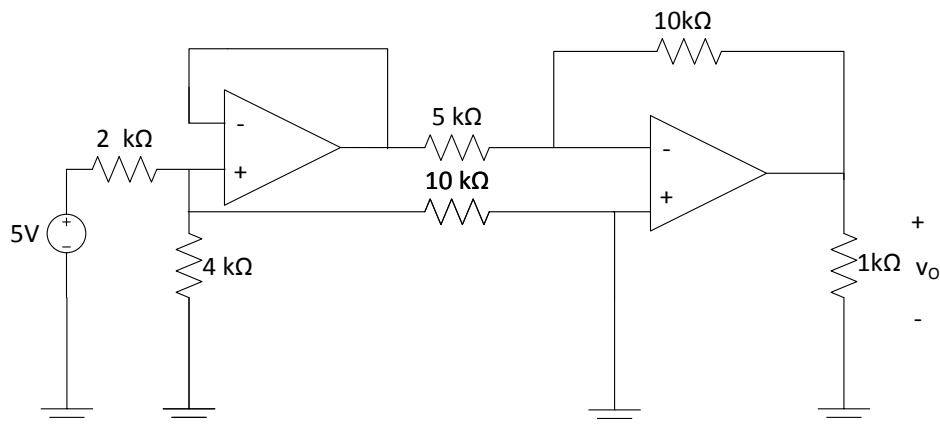


Figure 1

### Question 2 (10 points)

Considering the circuit shown in Figure 2, find the current  $i_x$  and the voltage  $v_x$ .

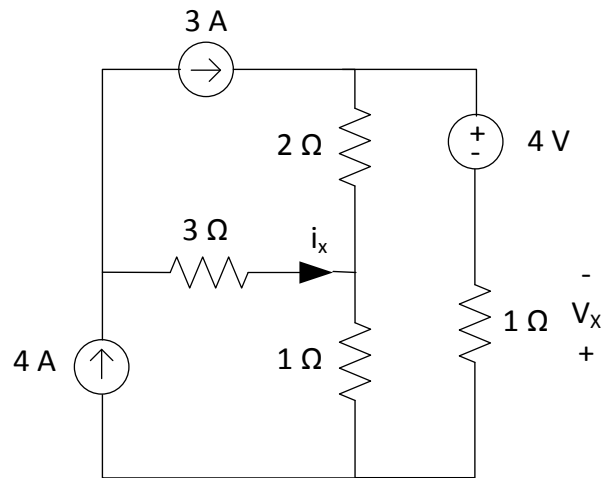


Figure 2

### Question 3 (15 points)

Considering the circuit shown in Figure 3,

- Find the value of  $\alpha$  which makes the Thévenin resistor shown through connectors **a** and **b** to be  $4\ \Omega$ .
- For the Thévenin resistor given in a), find the value of the load  $R_c$  that should be connected to connectors **a** and **b** in order to obtain a maximal power transfer through this load.
- Give the value of this maximal power.

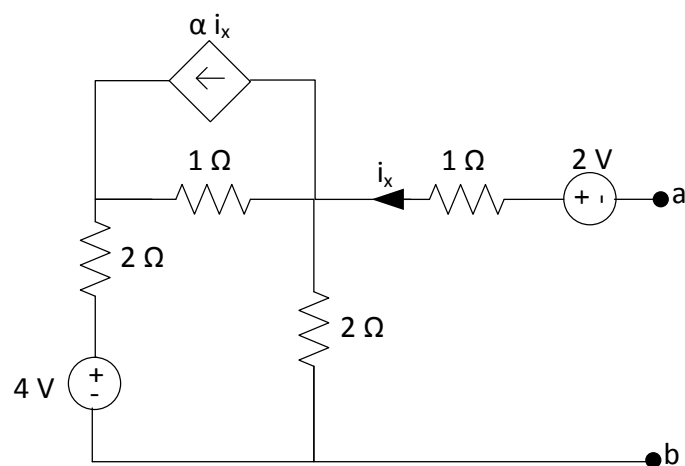


Figure 3

#### Question 4 (15 points)

Considering the circuit shown in Figure 4 where  $i_L(0) = -1$  A,

- Find the equation of  $i_L(t)$  for  $t \geq 0$ .
- Find the equation of  $V_L(t)$  for  $t \geq 0$ .

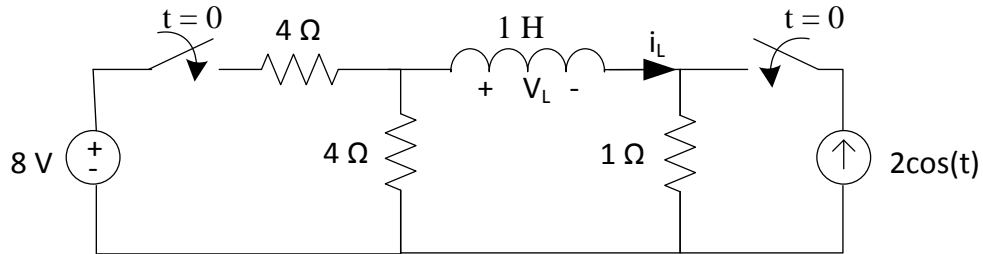


Figure 4

#### Question 5 (15 points)

Considering that for the circuit shown in Figure 5, the RMS voltage of the source ( $V_s$ ) is  $100\angle 0^\circ\text{V}$ ,

- Find the power factor (as seen by the source) and state whether it is lagging or leading.
- Find the value of the capacitance to connect between connectors **a** and **b** in order to obtain a unity power factor.

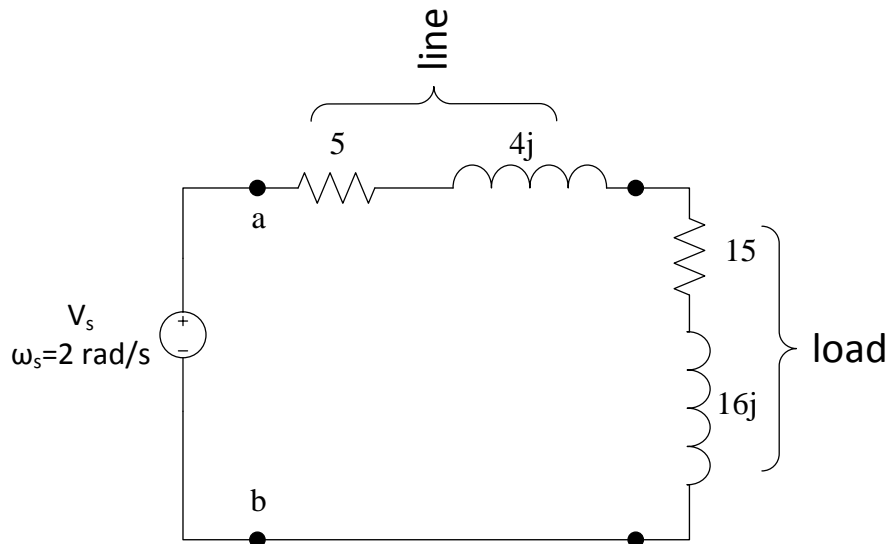


Figure 5

### Question 6 (20 points)

Considering the circuit shown in Figure 6,

- Draw the Thévenin equivalent circuit.
- Find the values of the components to connect between points **a** and **b** in order to maximize the average output power of this circuit.
- Give the value of this maximal average output power.

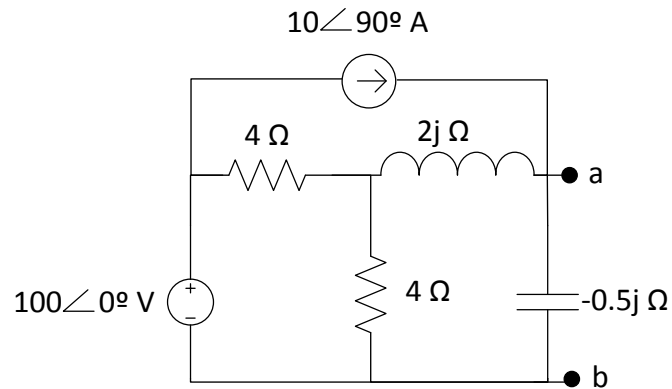


Figure 6

### Question 7 (15 points)

Find the voltage at node **V1** of the circuit shown in Figure 7.

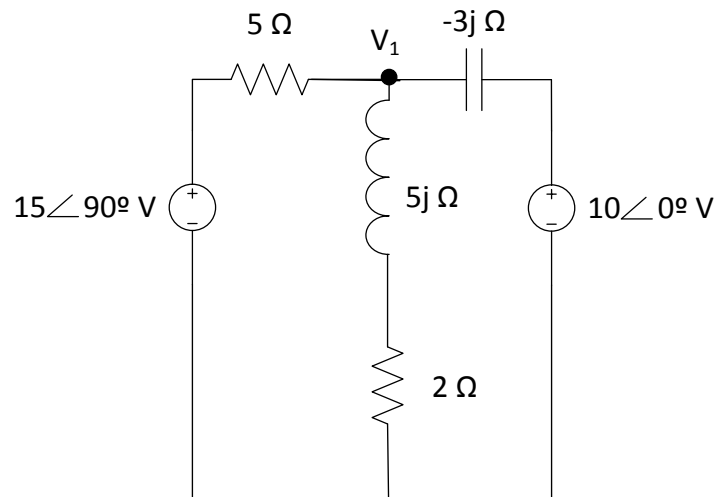


Figure 7