

ORDRE DES INGÉNIEURS DU QUÉBEC

MAY 2019 SESSION

Open-book examination
Calculators : only authorized models
Duration : 3 hours

16-EL-A1-CIRCUITS

Question 1 (15 points)

For the circuit shown in Figure 1, considering that the ideal operational amplifier operates in its linear region and that the capacitor is totally discharged initially,

- Find the expression of the transfer function $H(s) = V_L(s)/V_i(s)$
- Considering that $R = 50\ \Omega$, $R_1 = 30\ \Omega$, $R_2 = 100\ \Omega$, $R_3 = 150\ \Omega$, $C = 1\text{mF}$, $R_L = 15\ \Omega$ and the output current in steady state is $i_L(t) = 10 \sin(300t + 48^\circ)$, find the input voltage $v_i(t)$.

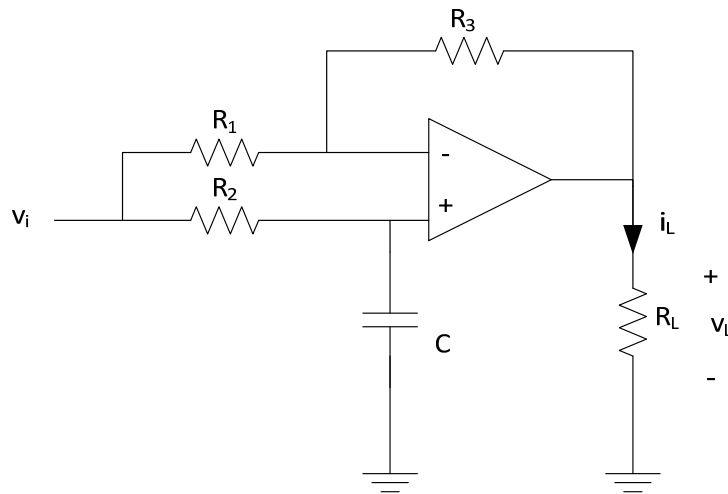


Figure 1

Question 2 (15 points)

Calculate the voltage at nodes v_1 and v_2 in the circuit shown in Figure 2.

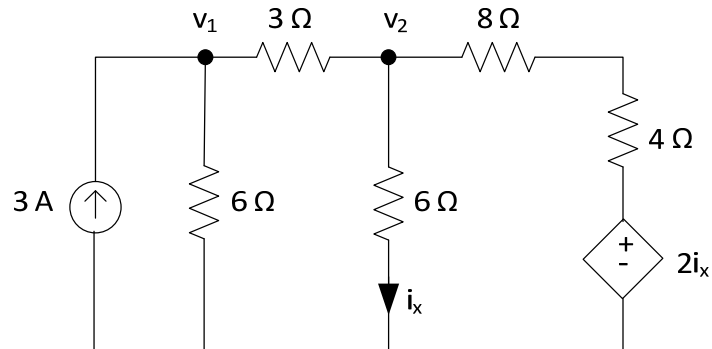


Figure 2

Question 3 (10 points)

For the circuit shown in Figure 3,

- Draw the equivalent Norton circuit.
- Draw the equivalent Thevenin circuit.

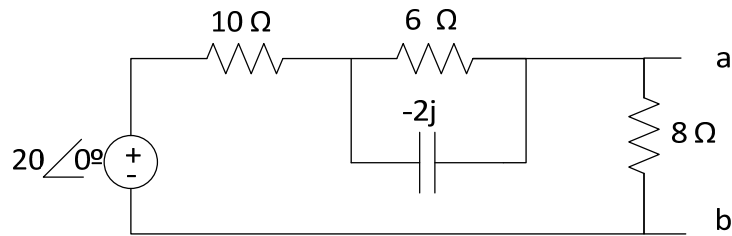


Figure 3

Question 4 (15 points)

For the circuit shown in Figure 4 where $I = 50 \text{ mA}$, $C = 250 \text{ } \mu\text{F}$, $L = 4 \text{ mH}$, $R_1 = 300 \text{ } \Omega$, $R_2 = 600 \text{ } \Omega$ and where no energy is stored initially,

- Provide the equation of the current $i_L(t)$ for $t \geq 0$.
- Provide the equation of $v(t)$ for $t \geq 0$?
- Which step response of Figure 5 corresponds to the current $i_L(t)$ once the switch is closed?
- Is it possible to obtain a circuit which behaves like a critically damped system by only changing the value of the resistor R_2 ? If so, what would be this value of R_2 ? If not, justify your answer by appropriate calculations.

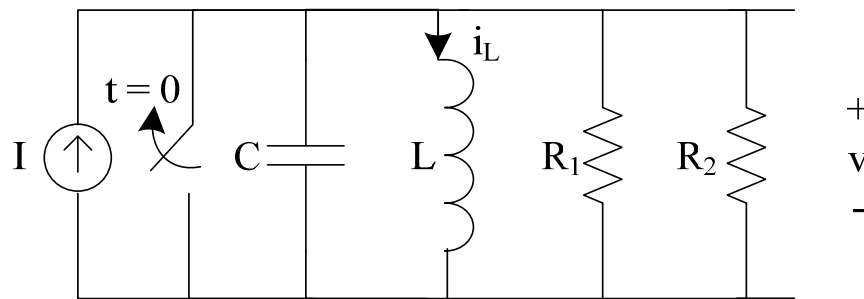


Figure 4

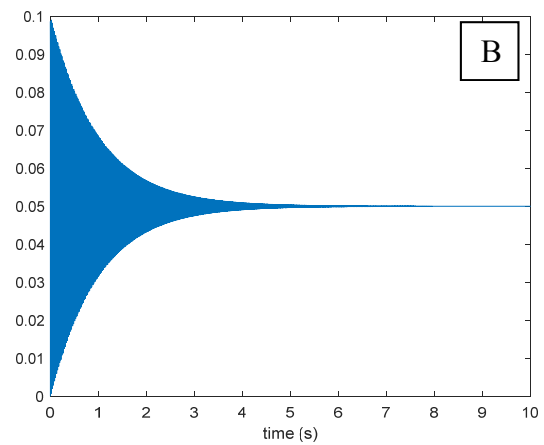
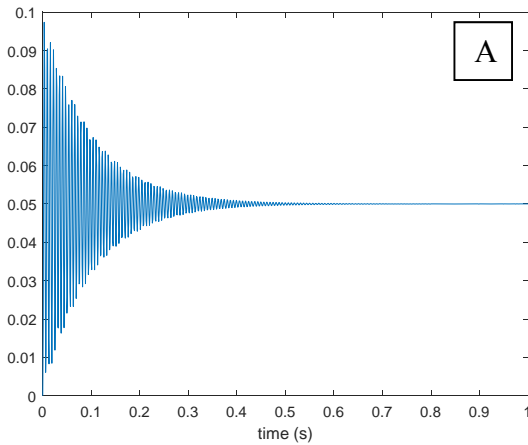


Figure 5

Question 5 (20 points)

Considering that for the circuit shown in Figure 6,

- The RMS voltage of the source (V_s) is $100\angle 0^\circ$ V
- $L_1 = 4j$;
- $R_2 = 35\ \Omega$;
- $L_2 = 26j$;
- The source provides a reactive power of 120 VAR ;
- The average power and the reactive power provided to the load are respectively 140 W and 104 VAR ;

- Calculate the value of the resistor R_1 in the line.
- Calculate the average power lost in the transmission line.

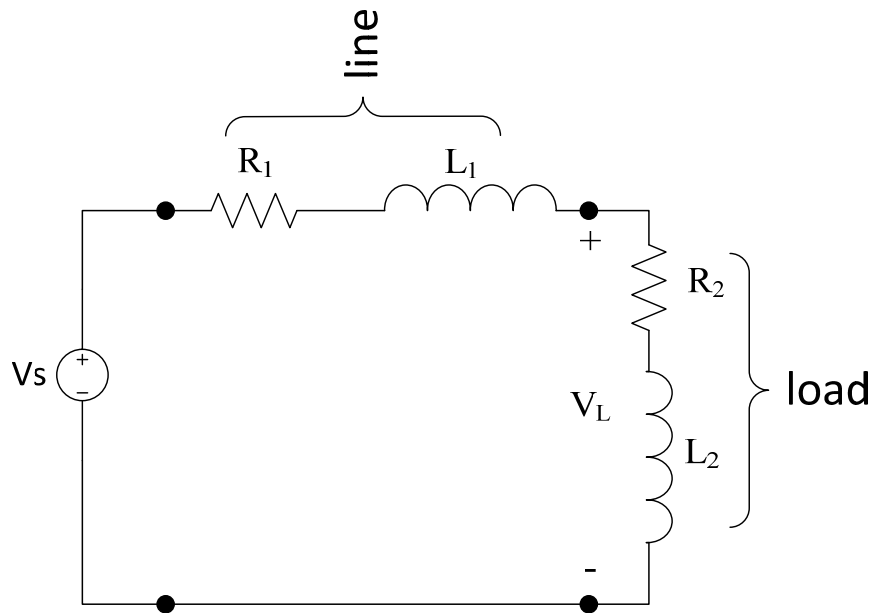


Figure 6

Question 6 (10 points)

For the circuit shown in Figure 7,

- Provide the Thevenin equivalent circuit.
- What would be the values of the resistor and the capacitor to connect between ports a and b in order to maximize the average power at the output of the circuit?
- Calculate this maximal average power.

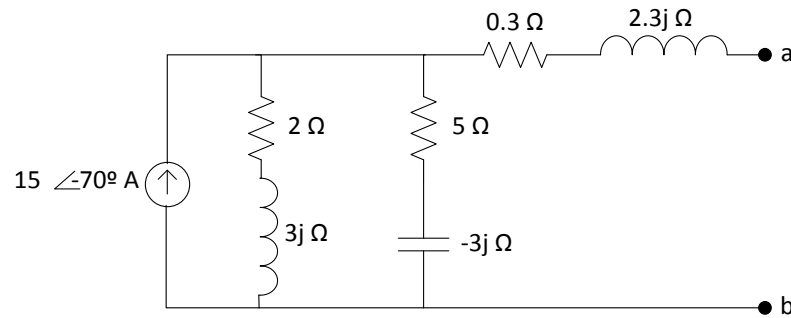


Figure 7

Question 7 (15 points)

For the circuit shown in Figure 8,

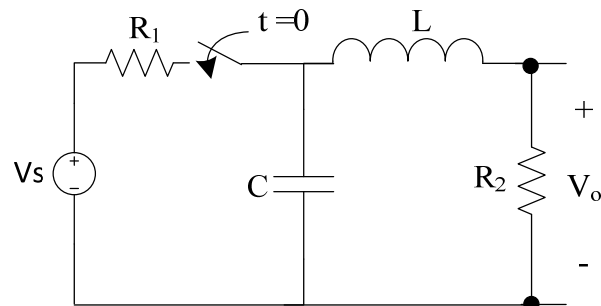


Figure 8

- Considering that the voltage in the capacitor and the current in the inductor are both zero for $t < 0$, find the expression of the transfer function $H(s) = \frac{V_o(s)}{V_s(s)}$ which describes the behavior of the circuit once the switch is closed.
- At $t = 0$, the switch is closed and the input voltage (V_s) is 10V with $R_1 = 5 \Omega$, $R_2 = 15 \Omega$, $C = 5\text{mF}$ and $L = 5\text{mH}$. What will be the final value of the output voltage (V_o)?
- What is the value of the current in the inductor at $t = 0^+$?
- What is the value of the current in the capacitor at $t = 0^+$?