

ORDRE DES INGÉNIEURS DU QUÉBEC

MAY 2020 SESSION

Open-book examination  
Calculators: only authorized models  
Duration: 3 hours

14-IF-A1 ELECTRONICS

## QUESTION 1 (20 points)

For the circuit in Figure 1,  $V_1 = 0\text{ V}$ ,  $V_2 = 25\text{ V}$ ,  $V_3 = 5\text{ V}$ ,  $V_4 = 40\text{ V}$ ,  $R_1 = R_2 = 1\text{ k}\Omega$  and  $R_3 = 20\text{ k}\Omega$ .

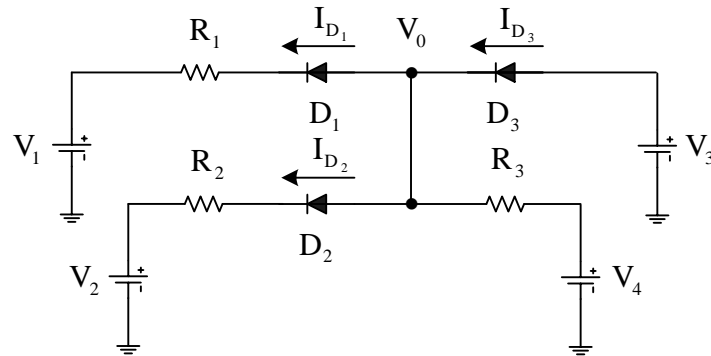


Figure 1

Find the values of  $I_{D_1}$ ,  $I_{D_2}$ ,  $I_{D_3}$  and  $V_0$ :

- When the diodes ideal ( $V_D = 0\text{ V}$ ) (10 points)
- When  $V_D = 0.7\text{ V}$ . (10 points)

## QUESTION 2 (20 points)

For the circuit of Figure 2,  $V = 5\text{ V}$ ,  $R_1 = 10\text{ k}\Omega$ ,  $R_2 = 10\text{ k}\Omega$ ,  $V_{D_1} = V_{D_2} = 0.7\text{ V}$  and

$$v_i = 20\sin(2\pi\frac{t}{T})\text{ V} :$$

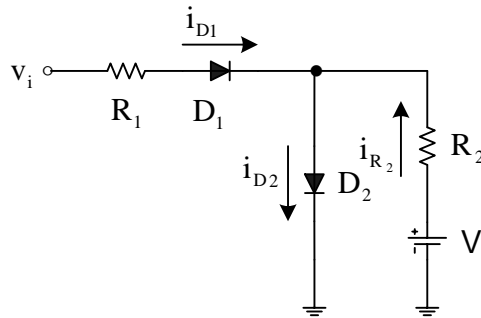


Figure 2

Find and sketch the currents  $i_{D_1}$  and  $i_{D_2}$  for  $0 \leq t \leq T$ . (20 points)

### QUESTION 3 (20 points)

For the circuit in Figure 3, assuming the ideal operational amplifier,  $R_1 = R_2 = R_3 = R_4 = R_5 = 10 \text{ k}\Omega$  and  $C_1 = C_2 = 0.1 \text{ }\mu\text{F}$  :

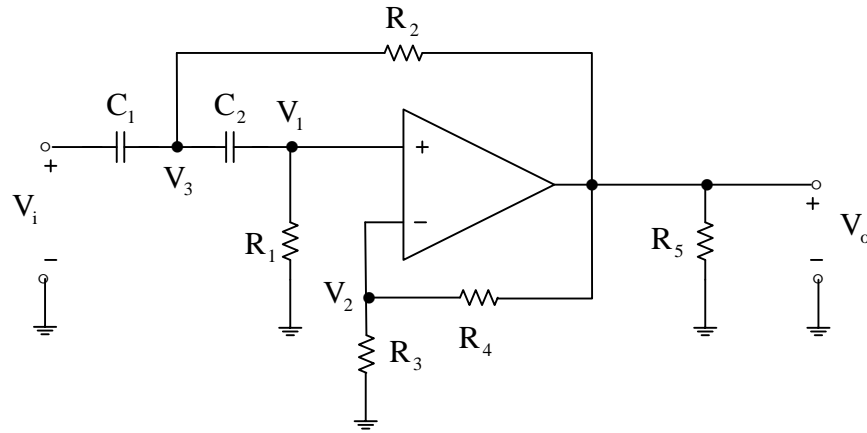


Figure 3

Find the gain  $\frac{V_o}{V_i}$ . (20 points)

### QUESTION 4 (20 points)

For the circuit in Figure 4,  $R_1 = R_3 = 6.8\text{k}\Omega$ ,  $R_2 = R_4 = 56\text{k}\Omega$ ,  $R_{C1} = R_{C2} = 2\text{k}\Omega$ ,  $R_{E1} = R_{E2} = R_{E3} = R_{E4} = 120\Omega$ ,  $R_L = 5.6\text{k}\Omega$ ,  $V_{BE} = 0.7\text{ V}$ ,  $V_{CC} = 12\text{ V}$ ,  $V_T = 26\text{ mV}$  and  $\beta = 100$  :

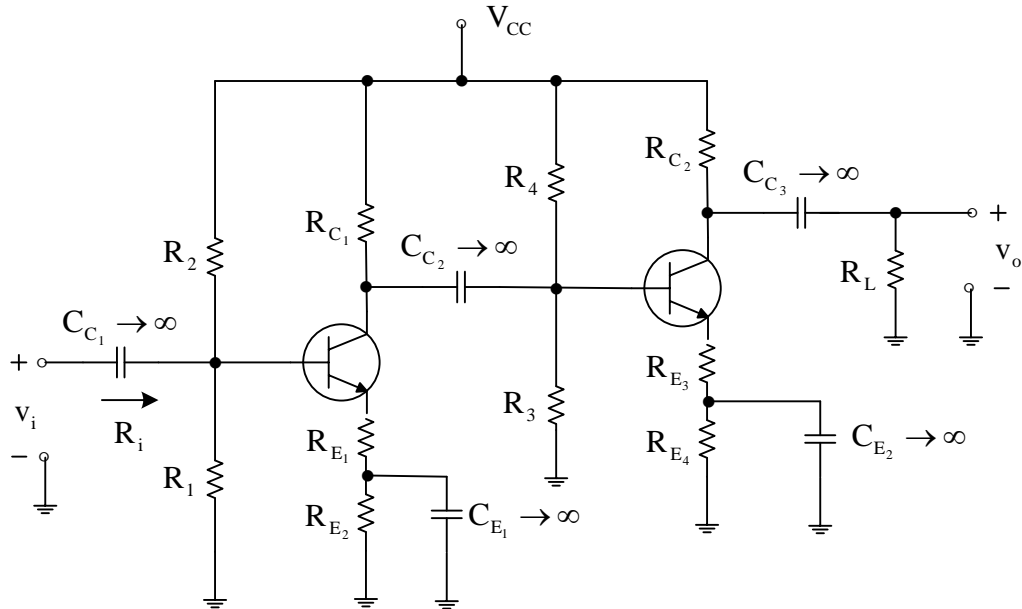


Figure 4

- Find  $I_{CQ}$  and  $V_{CEQ}$  for each transistor. (8 points)
- Find  $A_v = \frac{v_o}{v_i}$  and  $R_i$ . (12 points)

### QUESTION 5 (20 points)

For the circuit in Figure 5,  $R_1 = 1 \text{ M}\Omega$ ,  $R_S = 2.2 \text{ k}\Omega$ ,  $R_L = 2.2 \text{ k}\Omega$ ,  $V_p = -6 \text{ V}$ ,  $I_{DSS} = 10 \text{ mA}$ ,  $I_G \approx 0$ ,  $r_d \approx \infty$  and  $V_{DD} = 12 \text{ V}$  :

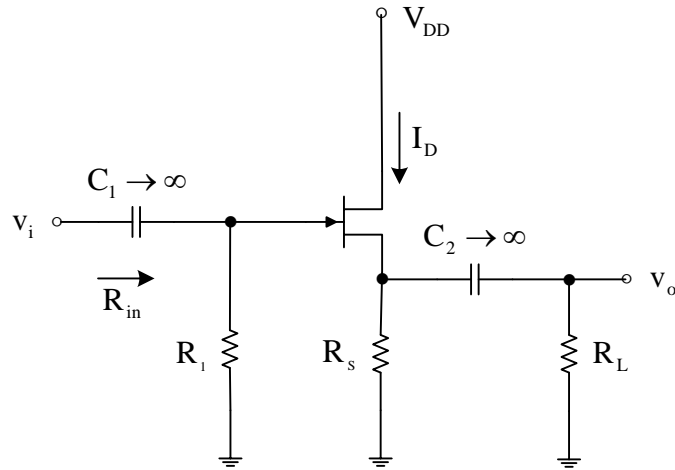


Figure 5

- Determine  $I_D$  and  $V_{DS}$ . (8 points)
- Determine the transconductance  $g_m$ . (4 points)
- Determine  $A_v = \frac{v_o}{v_i}$  and  $R_{in}$ . (8 points)