

ORDRE DES INGÉNIEURS DU QUÉBEC

NOVEMBER 2017 SESSION

Open-book examination  
Calculators: only authorized models  
Duration: 3 hours

14-IF-A1 ELECTRONICS

### QUESTION 1 (20 points)

For the circuit in Figure 1,  $V_{D1} = V_{D2} = 0.7 \text{ V}$ ,  $V_1 = 5 \text{ V}$  and  $V_2 = 5 \text{ V}$ .

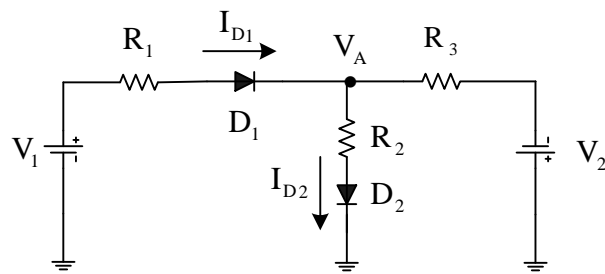


Figure 1

Find the values of  $V_A$ ,  $I_{D1}$  and  $I_{D2}$ :

- When  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 5 \text{ k}\Omega$  and  $R_3 = 5 \text{ k}\Omega$ . (10 points)
- When  $R_1 = 5 \text{ k}\Omega$ ,  $R_2 = 5 \text{ k}\Omega$  and  $R_3 = 10 \text{ k}\Omega$ . (10 points)

## QUESTION 2 (20 points)

For the circuit of Figure 2,  $V = 3\text{ V}$ ,  $R_1 = 10\text{ k}\Omega$ ,  $R_2 = 10\text{ k}\Omega$ ,  $V_D = 0.7\text{ V}$  and

$$v_i = 15 \sin(2\pi \frac{t}{T})\text{ V} :$$

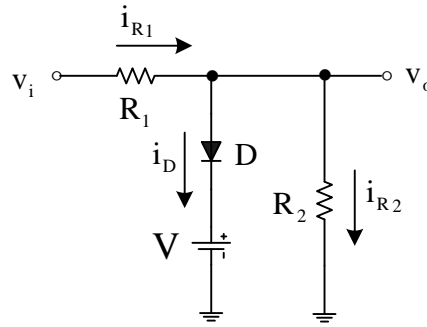


Figure 2

- Find and sketch the voltage  $v_o$  for  $0 \leq t \leq T$ . (10 points)
- Find and sketch the current  $i_D$  for  $0 \leq t \leq T$ . (10 points)

### QUESTION 3 (20 points)

For the circuit in Figure 3,  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ ,  $R_3 = 5 \text{ k}\Omega$ ,  $R_4 = 0.5 \text{ k}\Omega$ ,  $R_5 = 9.5 \text{ k}\Omega$ ,  $C_1 = 0.1 \text{ }\mu\text{F}$ ,  $C_2 = 0.1 \text{ }\mu\text{F}$ ,  $C_3 = 0.2 \text{ }\mu\text{F}$  and assuming ideal operational amplifiers :

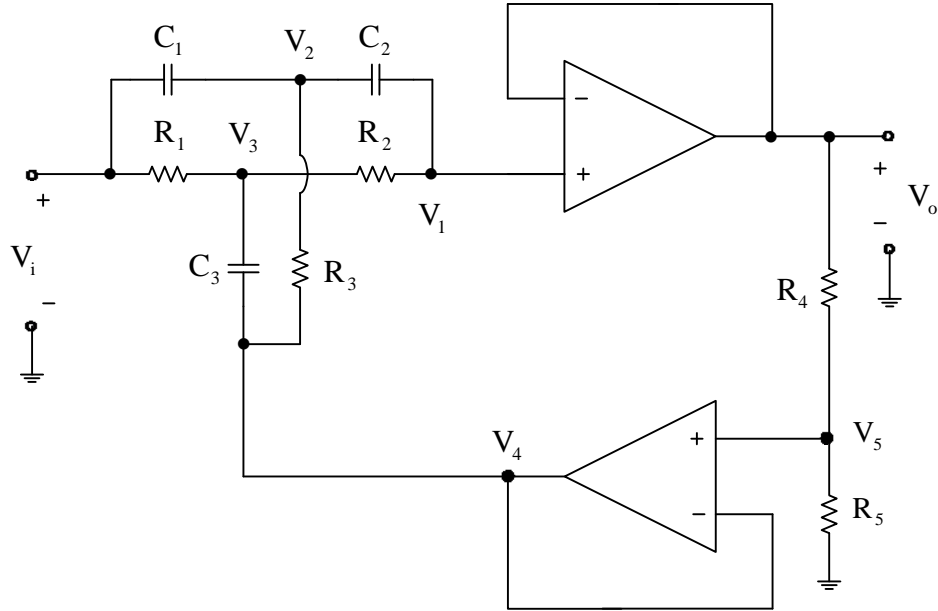


Figure 3

Find the gain  $\frac{V_o}{V_i}$ . (20 points)

### QUESTION 4 (20 points)

For the circuit in Figure 4,  $R_1 = 47 \text{ k}\Omega$ ,  $R_2 = 82 \text{ k}\Omega$ ,  $R_E = 1.5 \text{ k}\Omega$ ,  $R_L = 1.5 \text{ k}\Omega$ ,  $R_S = 10 \text{ k}\Omega$ ,  $V_{CC} = 12 \text{ V}$ ,  $V_{EB} = 0.7 \text{ V}$ ,  $\beta = 100$ ,  $V_T = 26 \text{ mV}$  and  $r_0 = \infty$  :

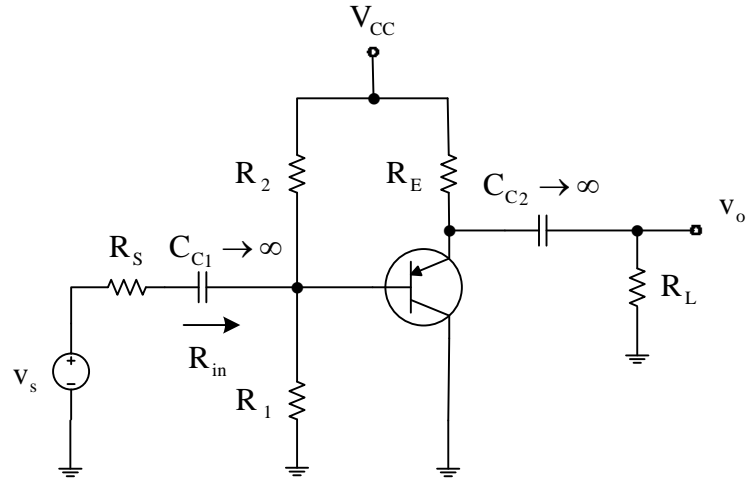


Figure 4

- Determine  $I_C$  and  $V_{EC}$ . (8 points)
- Determine  $R_{in}$  and  $A_v = \frac{v_o}{v_s}$ . (12 points)

### QUESTION 5 (20 points)

For the circuit in Figure 5,  $R_{\text{sig}} = 100\text{k}\Omega$ ,  $R_1 = 2\text{M}\Omega$ ,  $R_2 = 1\text{M}\Omega$ ,  $R_D = 150\ \Omega$ ,  $R_L = 1\text{k}\Omega$ ,  $V_t = 0.8\text{V}$ ,  $k_n = 12\text{mA/V}^2$  (NMOS 2N7000) and  $V_{DD} = 9\text{V}$  :

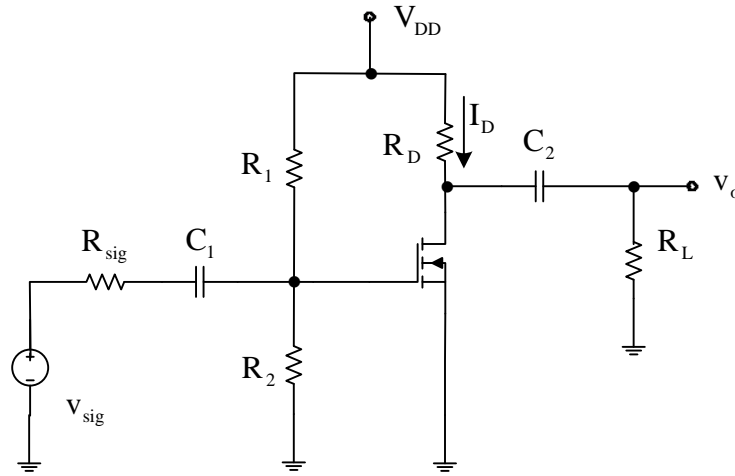


Figure 5

- Determine  $I_D$ ,  $V_{GS}$  and  $V_{DS}$ . (8 points)
- Determine the transconductance  $g_m$ . (4 points)
- Determine  $A_v = \frac{v_o}{v_{\text{sig}}}$ . (8 points)